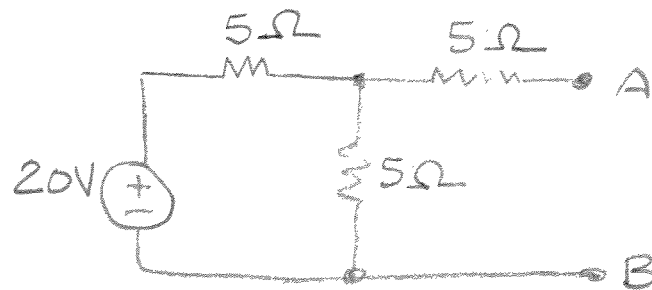


2/16/10

①




①

FIND THE THEVENIN VOLTAGE AND THE MAXIMUM POWER TRANSFER FOR THIS CIRCUIT.

- A. 20V $\frac{1}{3}$ 10.0W
 B. 20V $\frac{2}{3}$ 6.66W
 C. 10V $\frac{1}{3}$ 3.33W
 D. 5V $\frac{2}{3}$ 1.0W

②

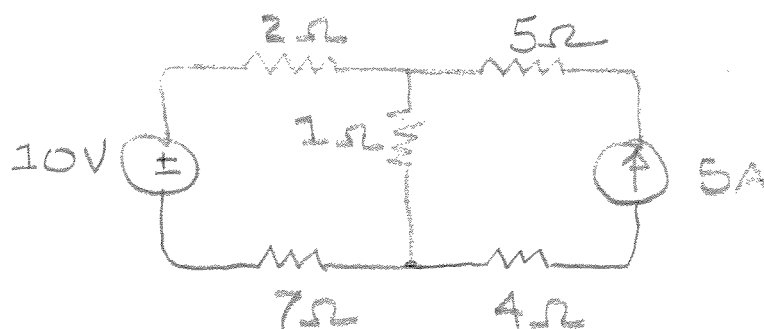

USE MESH ANALYSIS


FIND THE POWER SUPPLIED OR DISSIPATED BY THE 10V SOURCE.

- A. 10W SUPPLIED
 B. 5W SUPPLIED
 C. 5W DISSIPATED
 D. 2.5W DISSIPATED

2/16/10

(2)

(3)

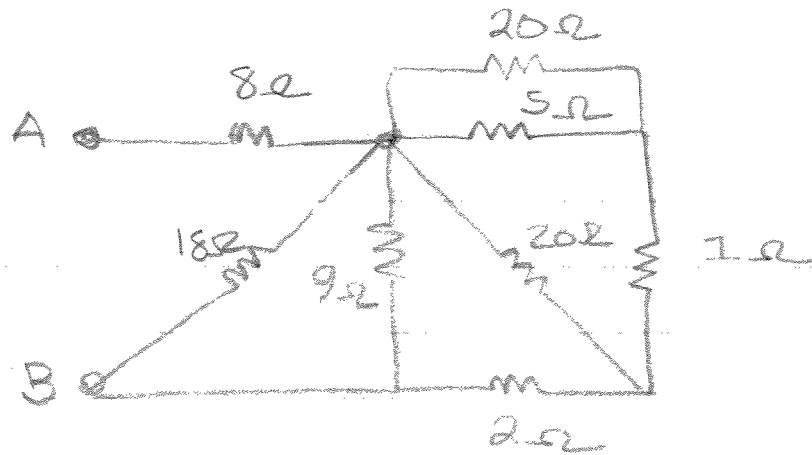

FIND THE EQUIVALENT RESISTANCE OF THIS CIRCUIT.

- A. 83Ω
- B. 65Ω
- C. 22Ω
- D. 11Ω

(4)

A SOLID COPPER CONDUCTOR AT 20°C HAS THE FOLLOWING CHARACTERISTICS.


RESISTIVITY = $1.77 \times 10^{-8} \Omega\text{m}$, diameter = 5mm, AND LENGTH = 5000m. WHAT IS THE RESISTANCE OF THE CONDUCTOR?

- A. 0.017Ω
- B. 4.5Ω
- C. 12Ω
- D. 18Ω

2/16/10

3

5

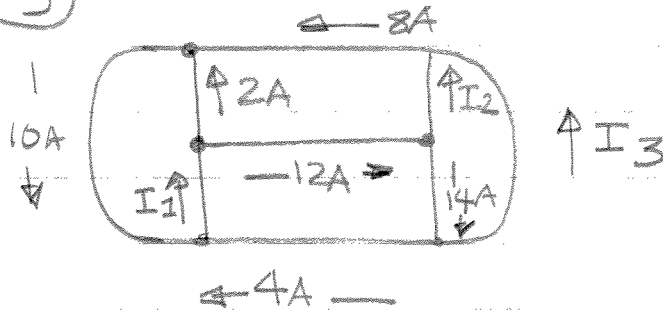

USE KCL TO FIND I_1 & I_2


A $14A$ & $2A$

B $-14A$ & $2A$

C $14A$ & $-2A$

D $10A$ & $-2A$

6

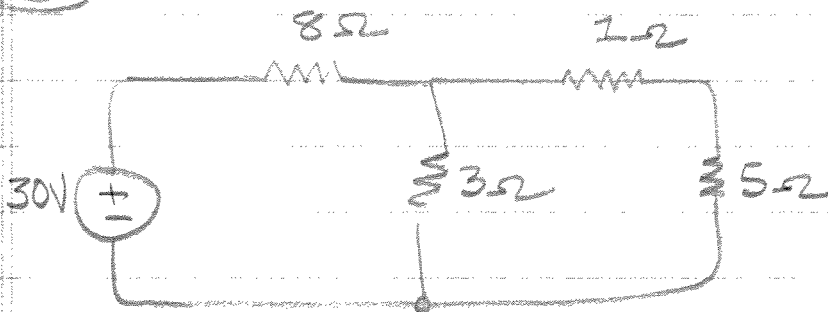

FIND THE CURRENT THROUGH THE 5Ω RESISTOR?

A. $4A$


B. $3A$

C. $2A$

D. $1A$


2/16/10

(4)

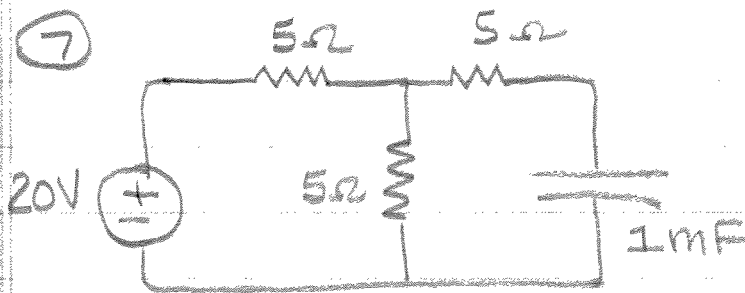


FIND THE ENERGY STORED IN THE 1mF CAPACITOR. THE CIRCUIT IS AT DC STEADY STATE.

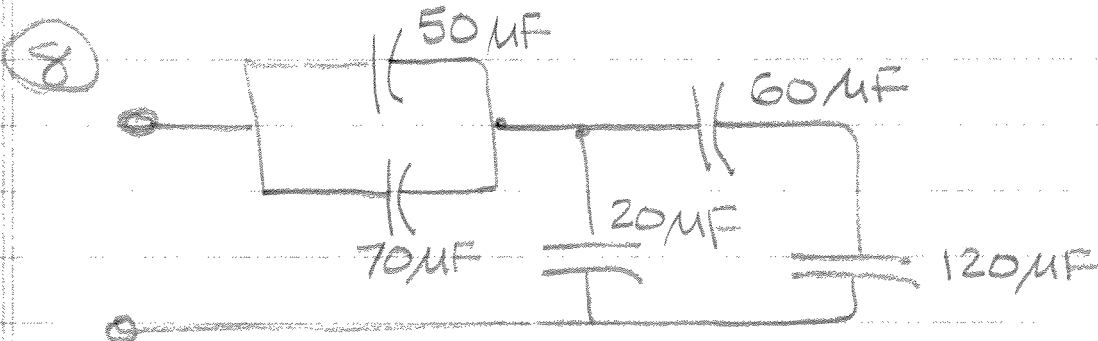- A. 200m Joules
- B. 67m Joules
- C. 50m Joules
- D. 100m Joules



FIND THE EQUIVALENT CAPACITANCE AT THE TERMINALS OF THE CIRCUIT.


- A. 20.9μF
- B. 40μF
- C. 120μF
- D. 320μF

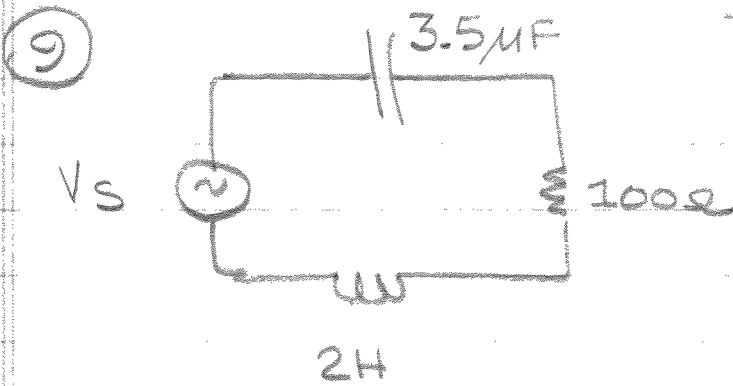AC CIRCUIT (5)

$$V_s = 100 \cos(377t - 90^\circ)$$

WHAT IS THE IMPEDANCE OF THIS AC CIRCUIT?

- A. $100 \Omega + 3.5 \mu F + 2 H$
- B. $100 + j377 \Omega$
- C. 100Ω
- D. $-j744 \Omega$

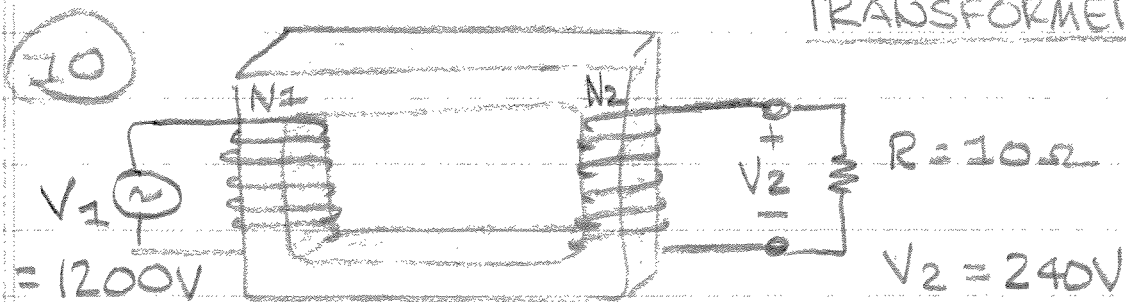TRANSFORMER

IF THE PRIMARY COIL, N_1 , OF THE TRANSFORMER HAS 500 TURNS, AND THE VOLTAGE ACROSS THE SECONDARY COIL IS 240V, HOW MANY TURNS DOES N_2 HAVE?

- A. 100 TURNS
- B. 200 TURNS
- C. 500 TURNS
- D. 1000 TURNS


2/16/10
CE MOCK F &
ANSWER KEY

2/16/09
6

- 1 10V $\frac{1}{2}$ 3.3W
- 2 5W
- 3 11 Ω
- 4 4.51 Ω
- 5 14A $\frac{1}{2}$ -2A
- 6 1A
- 7 50mJoules
- 8 40 μ F
- 9 100 Ω
- 10 100 TURNS

SEE PP. 7-12 FOR DETAILED
SOLUTIONS

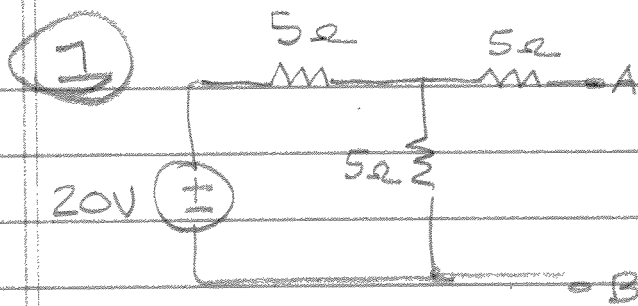THEVENIN EQUIVALENT CIRCUIT / MAX POWER TRANSFER



2/16/10


⑦

$$V_{TH} = V_{OC} = V_{5\Omega} \text{ (VERTICAL)}$$

VOLTAGE DIVISION:


$$V_{R1} = V_S \frac{R_1}{R_1 + R_2} = 20 \times \frac{5}{5+5} = 10V = V_{TH}$$
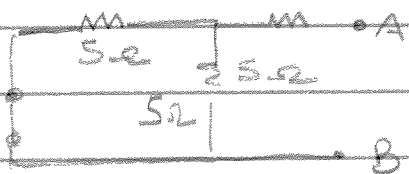
$$R_{LOAD} = R_{TH} \rightarrow \text{MAX POWER TRANSFER}$$



KILL SOURCE

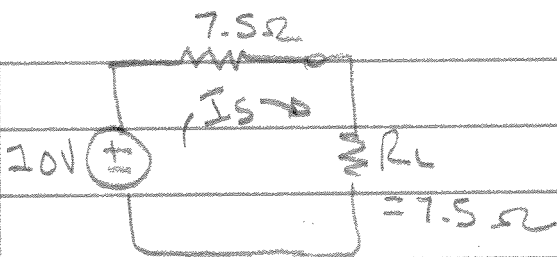
$$R_{TH} = 5 + 5 \parallel 5 = 7.5\Omega$$



$$I_S = \frac{10}{15} = 0.667A$$

THEVENIN EQUIVALENT CIRCUIT
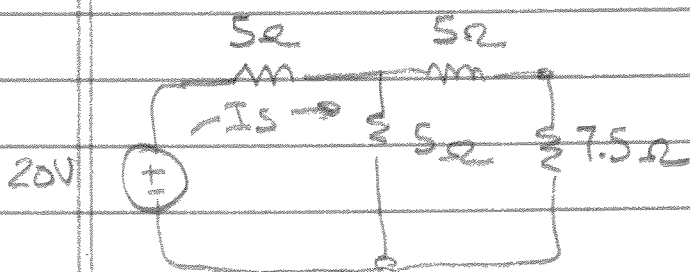
$$P_L = I^2 R = (0.667)^2 (7.5) = 3.33W$$



$$R_E = 5 + 5 \parallel 12.5 = 8.57\Omega$$

$$I_S = 20 / 8.57 = 2.33A$$

$$I_{LOAD} = 2.33 \times 5 / 7.5 = 0.667A$$

$$P_L = (0.667)^2 (7.5)$$


$$= 3.33W$$

CHECK

✓

2/16/10

8

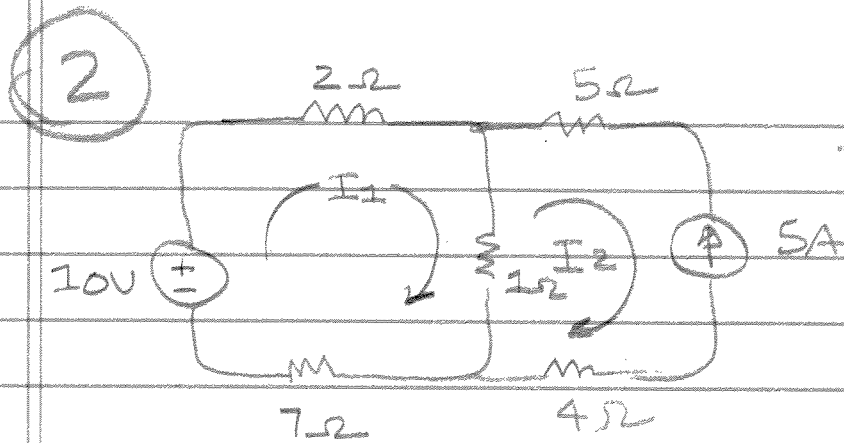

MESH # 1

$$-10 + 2I_1 + 1(I_1 - I_2) + 7I_1 = 0$$

$$-10 + 10I_1 - I_2 = 0$$

MESH # 2

$$I_2 = -5A$$

$$\therefore 10I_1 - (-5) - 10 = 0$$

$$10I_1 = 5 \quad \therefore I_1 = 0.5A$$

$$P_{10V} = IV = 0.5 \times 10 = 5W$$

KVL CHECK:


$$-10 + 2(0.5) + 1(0.5 - [-5]) + 7(0.5)$$

$$-10 + 1 + 5.5 + 3.5 = 0$$


EQUIVALENT RESISTANCE

2/16/10


3

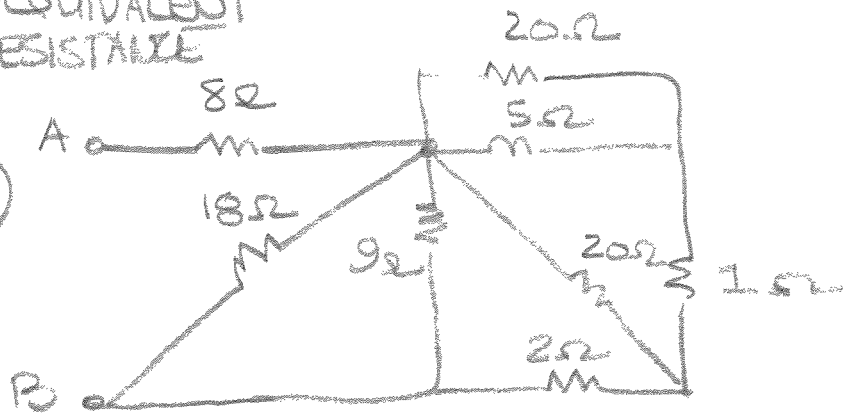
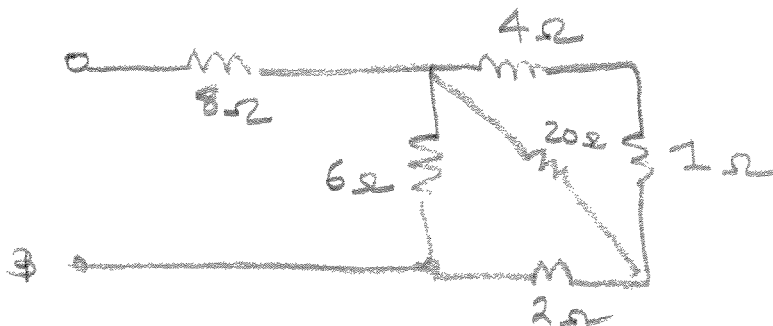
$$20 \parallel 5 = 4\Omega \quad \& \quad 18 \parallel 9 = 6\Omega$$



$$(4+1) \parallel 20 = 4\Omega$$

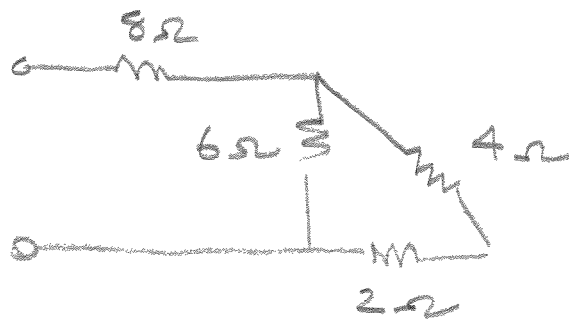

$$(2+4) \parallel 6 = 3\Omega \quad \& \quad 3+8 = 11\Omega$$


4 COPPER WIRE : USE $R = \rho L / A$

$$R = \frac{(1.77 \times 10^{-8} \Omega \cdot m)(5000m)}{\pi/4 \left[(5mm) \left(\frac{1m}{1000mm} \right) \right]^2} = 4.51\Omega$$

$$= 4.51\Omega$$

2/16/10
 (10)

(5)

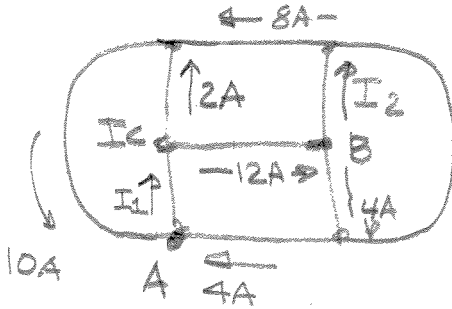


KCL
 $\sum I_{NODE} = 0$

$$\sum I_A = \underbrace{4 + 10}_{I_{in}} = \underbrace{I_1}_{I_{out}} = 14A = I_1$$

$$\sum I_B = 12 = \underbrace{14 + I_2}_{out}, \quad I_2 = -2A$$

$$\sum I_C = 14 = 2 + 12 \quad \checkmark$$

(6)

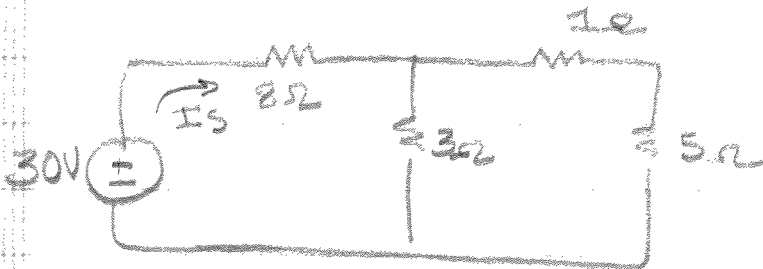

$$R_E = 8 + 3 \parallel 5 = 10 \Omega$$

$$I_S = 30 / 10 = 3A$$


$$I_{5\Omega} = I_{6\Omega} = 3 \times \frac{3}{9} = 1A$$

USE R_E ,
 OHMS LAW
 CURRENT DIVISION

2/16/10

(11)

7

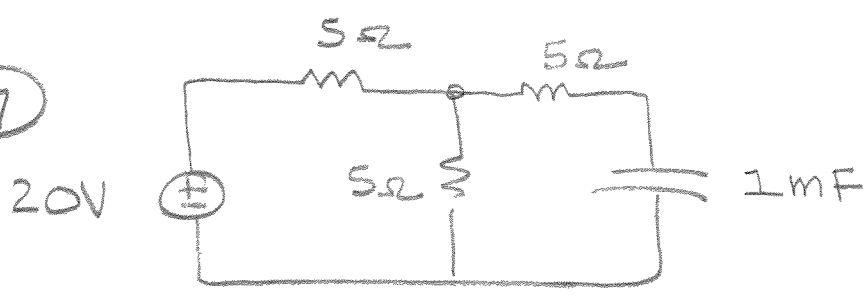


$$W_{CAP} = \frac{1}{2} CV^2$$

$$V_{CAP} = V_{5\Omega} = \frac{20 \times 5}{5 + 5} = 10V \quad \text{VOLTAGE DIV.}$$

NOTE, NO CURRENT FLOWS IN RIGHT LOOP, SO $V_{RIGHT} = 0$, $\therefore V_{CAP} = V_{5\Omega} = 10V$

$$W = \frac{1}{2} CV^2 = \frac{1}{2} (1 \times 10^{-3}) (10)^2 = 50mJoules$$

8

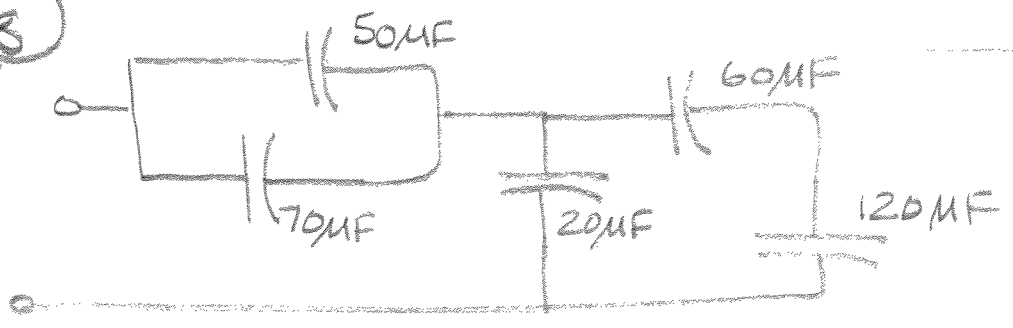

$$50\mu F \parallel 70\mu F = 120\mu F$$

$$60\mu F + 120\mu F = \frac{(60\mu F)(120\mu F)}{(60\mu F + 120\mu F)} = 40\mu F$$

$$40\mu F \parallel 20\mu F = 60\mu F$$


$$120\mu F + 60\mu F = \frac{(120\mu F)(60\mu F)}{(120 + 60)\mu F} = 40\mu F$$

2/16/10

(12)

$$100 \cos(377t - 90^\circ)$$

VOLTS

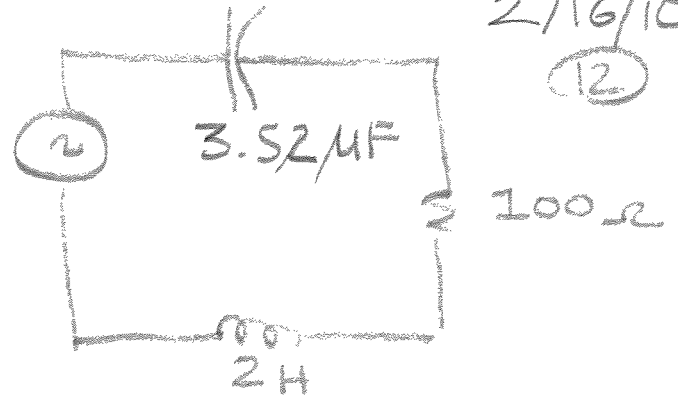

$$Z_R = 100 \Omega$$


$$Z_C = -\frac{j}{\omega C} = -\frac{j}{(377)(3.52 \times 10^{-6})} = -j754 \Omega$$

$$Z_L = j\omega L = j(377)(2) = +j754 \Omega$$

$$Z_{EQ} = 100 \Omega - j754 \Omega + j754 \Omega$$

$$= 100 \Omega$$

THIS IS CALLED A
RESONANT CIRCUIT

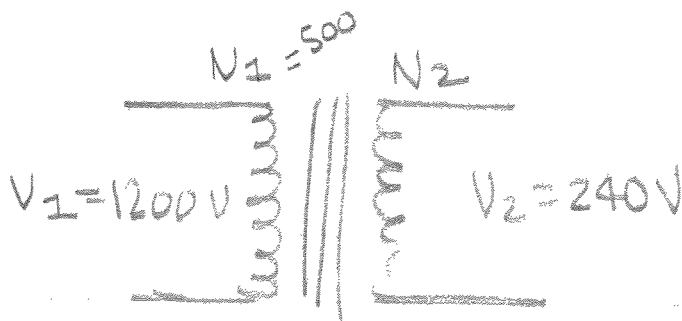

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} \quad \frac{240}{1200} = \frac{N_2}{500}$$

$$N_2 = 500 \left(\frac{240}{1200} \right) = 100 \text{ TURNS}$$